

Carry look Ahead Adder

- ↳ Carry depends on Sum ^(CLA)
- ↳ Speed than Full Adder
- ↳ Propagation delay of Full Adder is more
- ↳ Predict the Carry, which is predicted before.

A	B	Cin	Co
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$A \oplus B = 1$
 $Cin = 1$

$A \oplus B = 1, Cin = 0, Co = 0$

$A \oplus B = 1, Cin = 1$

If $A \oplus B$ is high
 Co is high.

$$C_0 = \underbrace{A \cdot B}_{\text{Carry generator}} + \underbrace{(A \oplus B) \cdot C_{in}}_{\text{Carry propagator}}$$

Carry generator

Carry propagator

Carry is generated due to $A \& B$


→ In this Carry C_0 is generated when C_{in} is propagated

G

P

$$C_0 = G + P C_{in}$$

$$C_{in} = G + P C_{in-1}$$

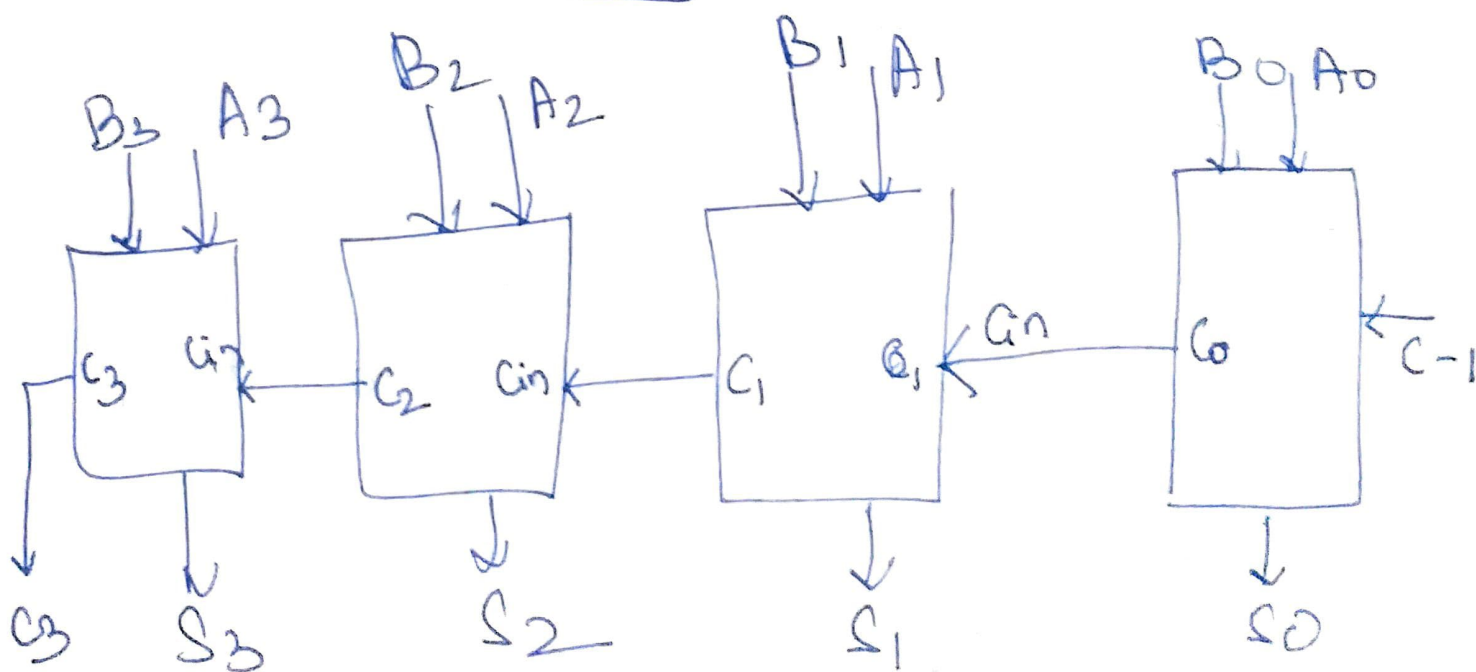

~~C_{in}~~ C_{-1} (Carry I/P) → C_0 (Carry O/P)

C_1 (Carry I/P) → C_2 (Carry O/P)

$C_{in-1} = C_0 =$

$$C_i = G_i + P_i C_{i-1}$$

$\left. \begin{array}{l} A \\ B \\ C_{i-1} \end{array} \right\}$ Calculate the sum & Carry

$$i = 0$$

$$C_0 = G_0 + P_0 C_{0-1} \Rightarrow C_0 = G_0 + P_0 C_{-1} \quad \text{--- (1)}$$

\searrow (A)

$$C_1 = G_1 + P_1 C_0 \quad \text{--- (2)}$$

$$C_1 = G_1 + P_1 (G_0 + P_0 C_{-1})$$

$$\boxed{C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{-1}} \rightarrow \text{(B)}$$

C_1 depends on C_{-1} , C_{-1} is our input so, it need not wait for the sum to get C_1

$$i = 2$$

$$C_2 = G_2 + P_2 C_1$$

Substitute C_1

$$C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_{-1})$$

$$\underline{\underline{C_2 = G_2 + P_2 G_1 + P_1 P_2 G_0 + P_1 P_2 P_0 C_{-1}}} \rightarrow \text{(C)}$$

↳ This helps save time.

↳ So if C_{-1} is there I can get any carry value.


$$i = 3$$

$$C_3 = G_3 + P_3 C_2$$

$$= G_3 + P_3 [G_2 + P_2 G_1 + P_1 P_2 G_0 + P_1 P_2 C_{-1}]$$

$$C_3 = G_3 + P_3 G_2 + P_2 P_3 G_1 + P_1 P_2 P_3 G_0 + \cancel{P_1 P_2 P_3} C_{-1}$$

↳ (AD)

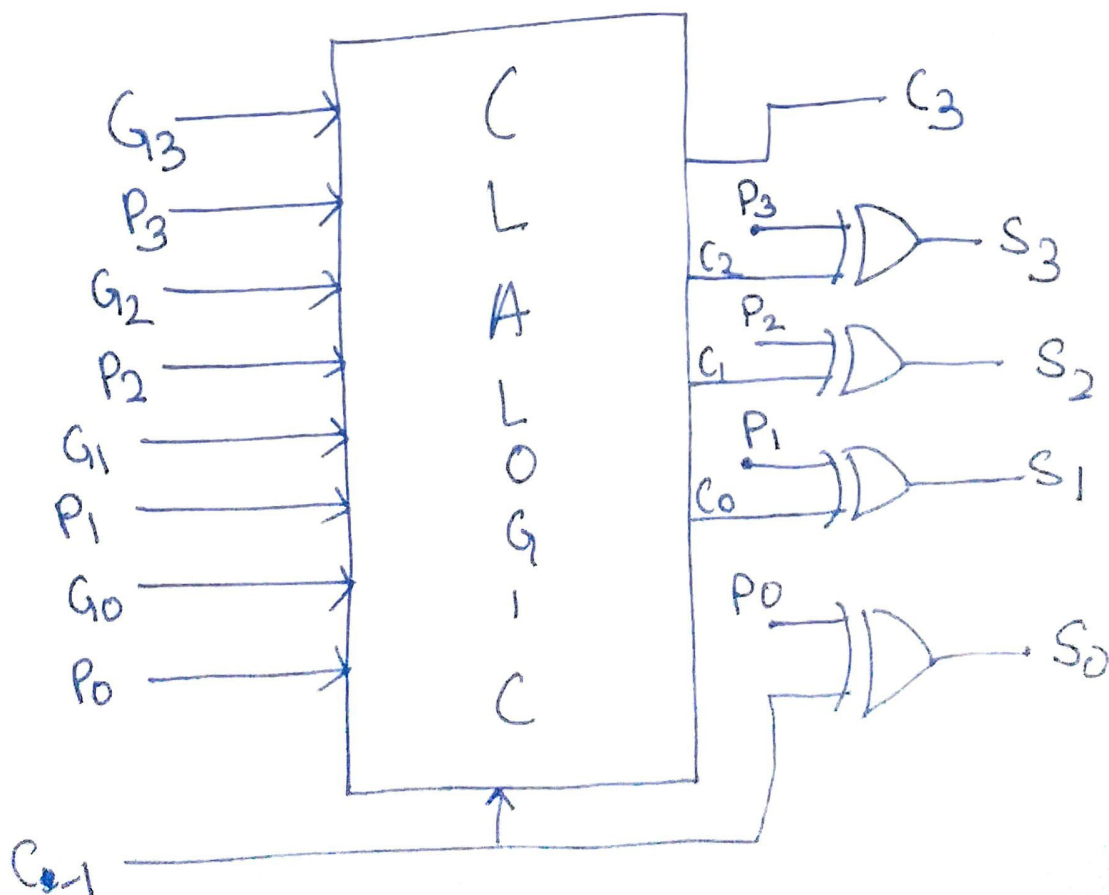

$$G_3 = A_3 \cdot B_3$$

$$P_3 = A_3 \oplus B_3$$

$$G_2 = A_2 \cdot B_2$$

$$P_2 = A_2 \oplus B_2$$

$$G_1 = A_1 \cdot B_1$$

$$P_1 = A_1 \oplus B_1$$

$$G_0 = A_0 \cdot B_0$$

$$P_0 = A_0 \oplus B_0$$

$$S_3 = \underbrace{A_3 \oplus B_3}_{P_3} \oplus G_2$$