

Simplify the following expression using
Boolean algebra

$$(1) Z = AB + A(B+C) + B(B+C)$$

$$= AB + AB + AC + BB + BC$$

$$= AB + AC + B + BC$$

$$= AB + AC + B(1+C)$$

$$= AB + AC + B$$

$$= B + AB + AC$$

$$= B(1+A) + AC$$

$$\boxed{Z = B + AC} \quad \underline{\text{ANS}}$$

$$AB + AB = AB$$

$$B.B = B$$

$$1 + C = 1$$

$$1 + A = 1$$

$$(2) Y = ABC + A\bar{B}C + AB\bar{C}$$

$$= AC(B + \bar{B}) + AB\bar{C}$$

$$= AC + AB\bar{C}$$

$$= A(C + B\bar{C})$$


$$= A(C + B)$$

$$\boxed{Y = A(B+C)} \quad \underline{\text{ANS}}$$


$$B + \bar{B} = 1$$

$$C + B\bar{C} = C + B$$

①

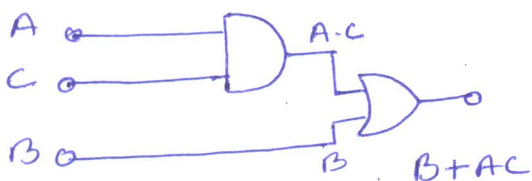

②

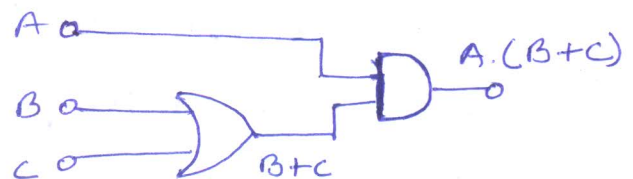

$$\begin{aligned}
 (3) \quad Z &= AB + ABC + \bar{A}B + A\bar{B}C \\
 &= AB + \bar{A}B + ABC + A\bar{B}C \\
 &= B(A + \bar{A}) + AC(B + \bar{B})
 \end{aligned}$$

$$Z = B + AC$$

$$\begin{aligned}
 A + \bar{A} &= 1 \\
 B + \bar{B} &= 1
 \end{aligned}$$


$$(4) \quad Z = AB + AC + B\bar{C}$$

$$\begin{aligned}
 &= AB(C + \bar{C}) + AC + B\bar{C} \\
 &= ABC + AB\bar{C} + AC + B\bar{C} \\
 &= ABC + AC + AB\bar{C} + B\bar{C} \\
 &= AC(B + 1) + B\bar{C}(A + 1)
 \end{aligned}$$

$$C + \bar{C} = 1$$

$$Z = AC + B\bar{C}$$

ANS

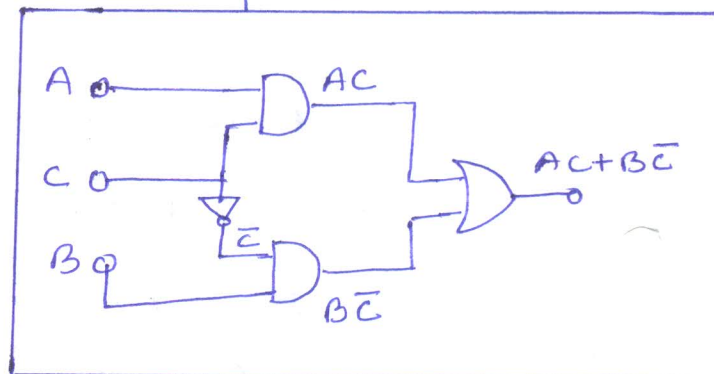

$$\begin{aligned}
 A + 1 &= 1 \\
 B + 1 &= 1
 \end{aligned}$$

$$\begin{aligned}
 (5) \quad Z &= (A + B)(\bar{A} + C) \\
 &= A\bar{A} + AC + \bar{A}B + BC \\
 &= AC + \bar{A}B + BC
 \end{aligned}$$

$$\begin{aligned}
 &= AC + \bar{A}B + (A + \bar{A})BC \\
 &= AC + \bar{A}B + ABC + \bar{A}BC \\
 &= AC + ABC + \bar{A}B + \bar{A}BC \\
 &= AC(1 + B) + \bar{A}B(1 + C)
 \end{aligned}$$

$$A + \bar{A} = 1$$

$$1 + B = 1$$

$$1 + C = 1$$

$$Z = AC + \bar{A}B \quad \text{ANS}$$

Realize the following using NAND gates.

⑥ $Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B + \bar{B}\bar{C}$

$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B(C+\bar{C}) + (A+\bar{A})\bar{B}\bar{C}$$

$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$

$$= \bar{A}\bar{B}(C+\bar{C}) + \bar{A}B(\bar{C}+C) + A\bar{B}\bar{C}$$


$$= \bar{A}\bar{B} + \bar{A}B + A\bar{B}\bar{C}$$

$$= \bar{A}(\bar{B}+B) + A\bar{B}\bar{C}$$


$$\boxed{Z = \bar{A} + A\bar{B}\bar{C}} \quad \underline{\text{ANS}}$$

$$\begin{aligned} \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} &= \bar{A}\bar{B}\bar{C} \\ B + \bar{B} &= 1 \\ C + \bar{C} &= 1 \end{aligned}$$

using gates

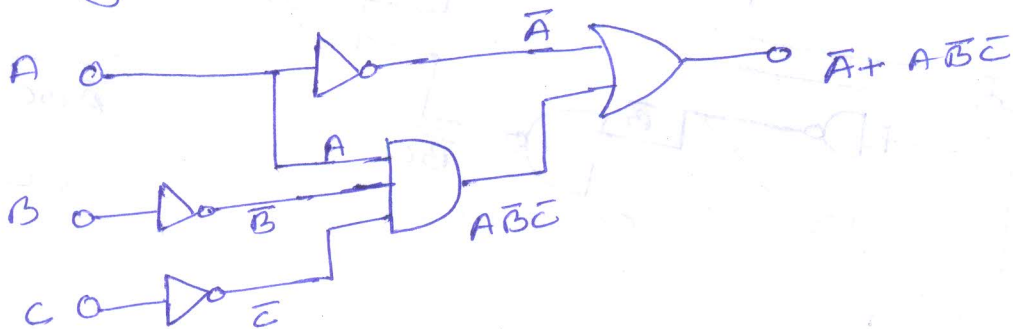

using NAND gate

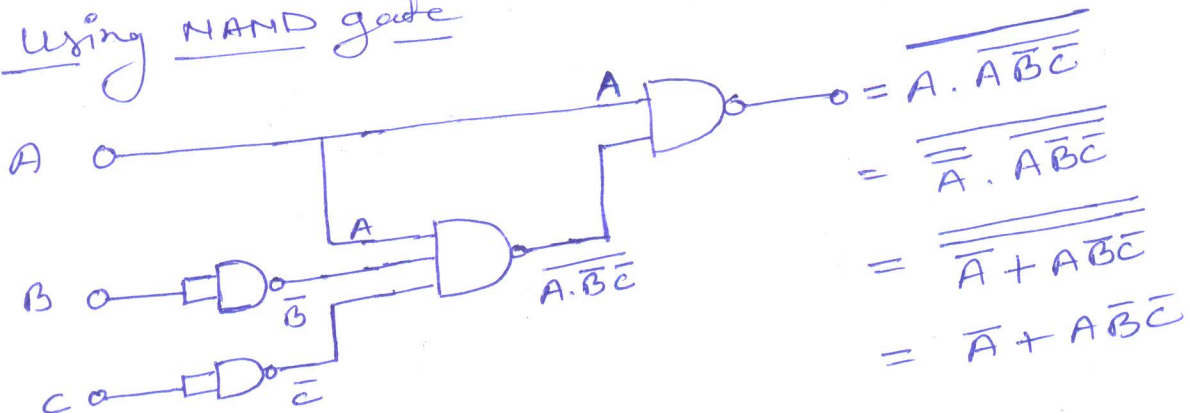

$$\textcircled{7} \quad Y = \bar{A}BC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$= \bar{A}BC + \bar{B}\bar{C}(\bar{A} + A)$$

$$\boxed{Y = \bar{A}BC + \bar{B}\bar{C}}$$


$$\bar{A} + A = 1$$

for realization using NAND gates

$$Y = \overline{\overline{\bar{A}BC + \bar{B}\bar{C}}}$$

$$= \overline{\bar{A}BC} \cdot \overline{\bar{B}\bar{C}}$$
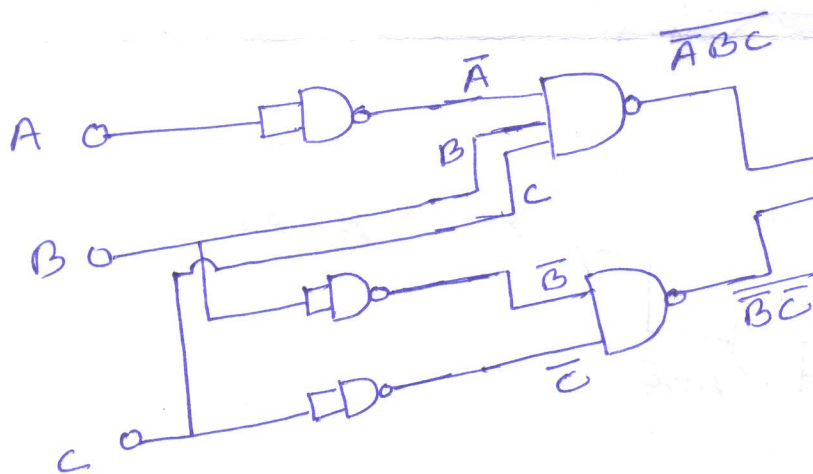
$$= \overline{\bar{A}BC} \cdot \overline{\bar{B}\bar{C}}$$




$$\begin{aligned} &= \overline{\bar{A}BC} \cdot \overline{\bar{B}\bar{C}} \\ &= \overline{\bar{A}BC + \bar{B}\bar{C}} \\ &= \bar{A}BC + \bar{B}\bar{C} \end{aligned}$$

⑧

$$Y = A\bar{B} + \bar{A}B = \text{XOR Gate using NAND}$$

$$= \overline{\overline{A\bar{B}} + \overline{\bar{A}B}}$$
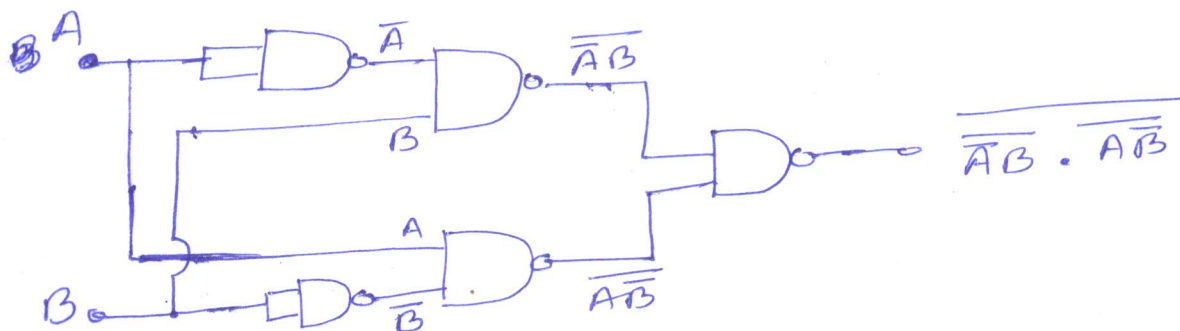
$$= \overline{\overline{A\bar{B}} \cdot \overline{\bar{A}B}}$$




⑨ ~~using~~ XOR using NOR gates

$$Y = A\bar{B} + \bar{A}B = \overline{\overline{A\bar{B}} + \overline{\bar{A}B}}$$

$$= \overline{\overline{A+B} + \overline{\bar{A}+\bar{B}}}$$
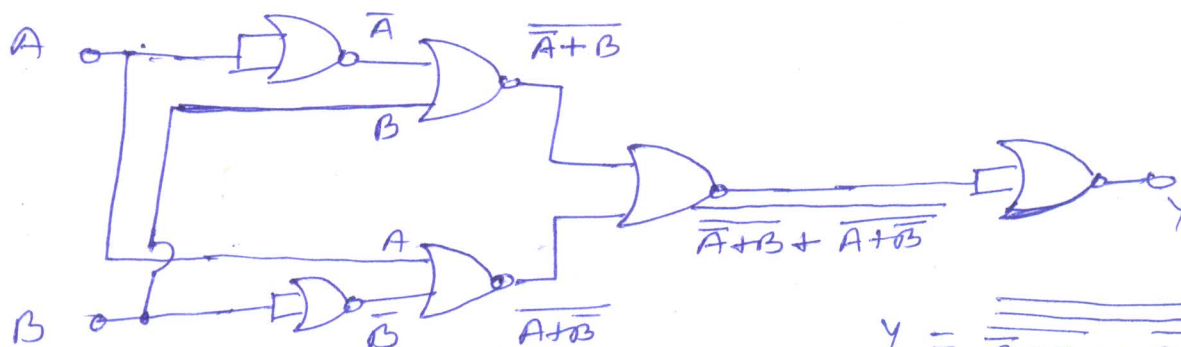
$$= \overline{\overline{A+B} + \overline{A+B}}$$



$$Y = \overline{\overline{A+B} + \overline{A+B}}$$

$$Y = \overline{\overline{A+B} + \overline{A+B}}$$

Standard Representations of Logical Functions :

1. Sum of Products (SOP)

$$\text{Ex. (i)} \quad AB + \bar{A}B + A\bar{B}$$

$$\text{(ii)} \quad AB + \bar{B}CD + AB\bar{C}$$

2. Product of Sum (POS)

$$\text{Ex. (i)} \quad (A + \bar{B})(A + B + C)(B + C)$$

$$\text{(ii)} \quad (\bar{A} + C)(\bar{B} + A)(A + \bar{B} + \bar{C})$$

Canonical forms :-

When each term of a logical expression contains all literals, it is called a canonical form of the logical variables. If each term in SOP and POS forms contains all the literals then these are known as canonical or standard SOP and POS forms respectively.

Each individual term in standard SOP form is called minterm and in standard POS form as maxterm.

Exp (1) Convert $A + A\bar{B}$ into standard SOP form.

$$\begin{aligned} A + A\bar{B} &= A(B + \bar{B}) + A\bar{B} \\ &= AB + A\bar{B} + A\bar{B} \\ &= AB + A\bar{B} \\ &\quad \downarrow \\ &\quad \text{minterm} \end{aligned}$$

(i) Convert $(A+B)(B+C)$ into standard POS form.

$$(A+B)(B+C) = (A+B+C\bar{C})(B+C+A\bar{A})$$

$$= (A+B+C)(A+B+\bar{C})(B+C+A)(B+C+\bar{A})$$

same

$$\begin{aligned} \because A+BC \\ &= (A+B)(A+C) \end{aligned}$$

$$= (A+B+C)(A+B+\bar{C})(A+B+C)(\bar{A}+B+C)$$

$$= (A+B+C)(A+B+\bar{C})(\bar{A}+B+C)$$

$$[\because A+A=A]$$

↓
maxterm

Minterm And Maxterm:-

$$Y = ABCD + A\bar{B}CD + A\bar{B}\bar{C}D + AB\bar{C}D$$

above expression can be expressed in the form of minterm.

$$Y = ABCD + A\bar{B}CD + A\bar{B}\bar{C}D + AB\bar{C}D$$

1 1 1 1	1 0 1 1	1 0 0 1	1 1 0 1
↓	↓	↓	↓
15	11	9	13
↓	↓	↓	↓
m_{15}	m_{11}	m_9	m_{13}

~~$Y = \Sigma m$~~


$$Y(A, B, C, D) = \Sigma m(9, 11, 13, 15)$$

Then the corresponding maxterm form is

$$Y(A, B, C, D) = \Pi M(0, 1, 2, 3, 4, 5, 6, 7, 8, 10, 12, 14)$$

Maxterm conversion can be done by given method.
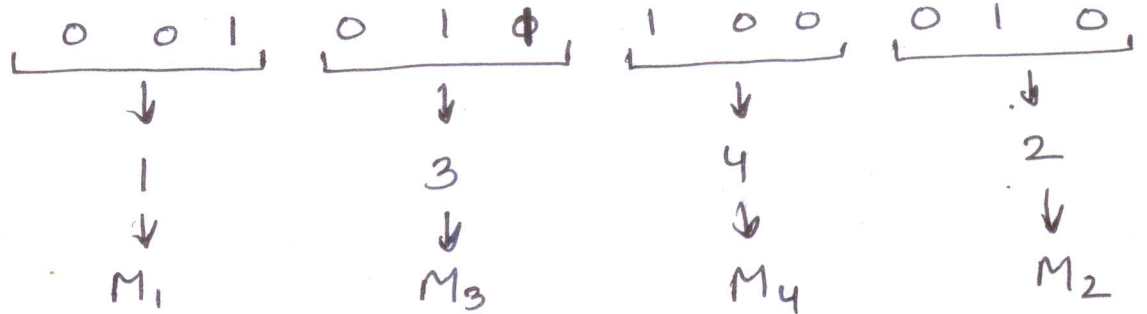
$$Y = (A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+B+C)(A+\bar{B}+C)$$




$$Y(A,B,C) = \prod M(1, 2, 3, 4)$$

then minterm form is

$$Y(A,B,C) = \sum m(0, 5, 6, 7)$$


Karnaugh Maps

(1) $Y(A, B, C) = \sum m(0, 2, 4, 5, 6)$

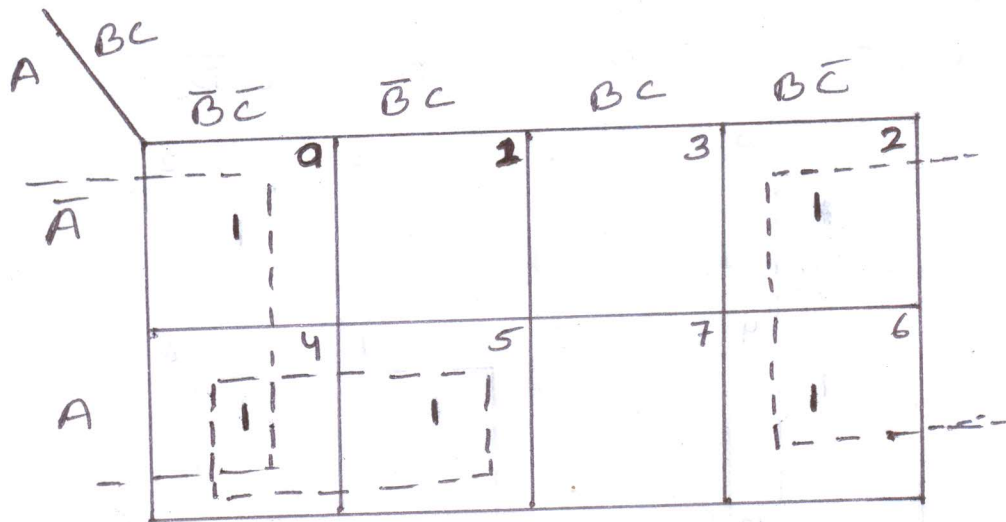

$Y = \overline{C} + A\overline{B}$ Ans

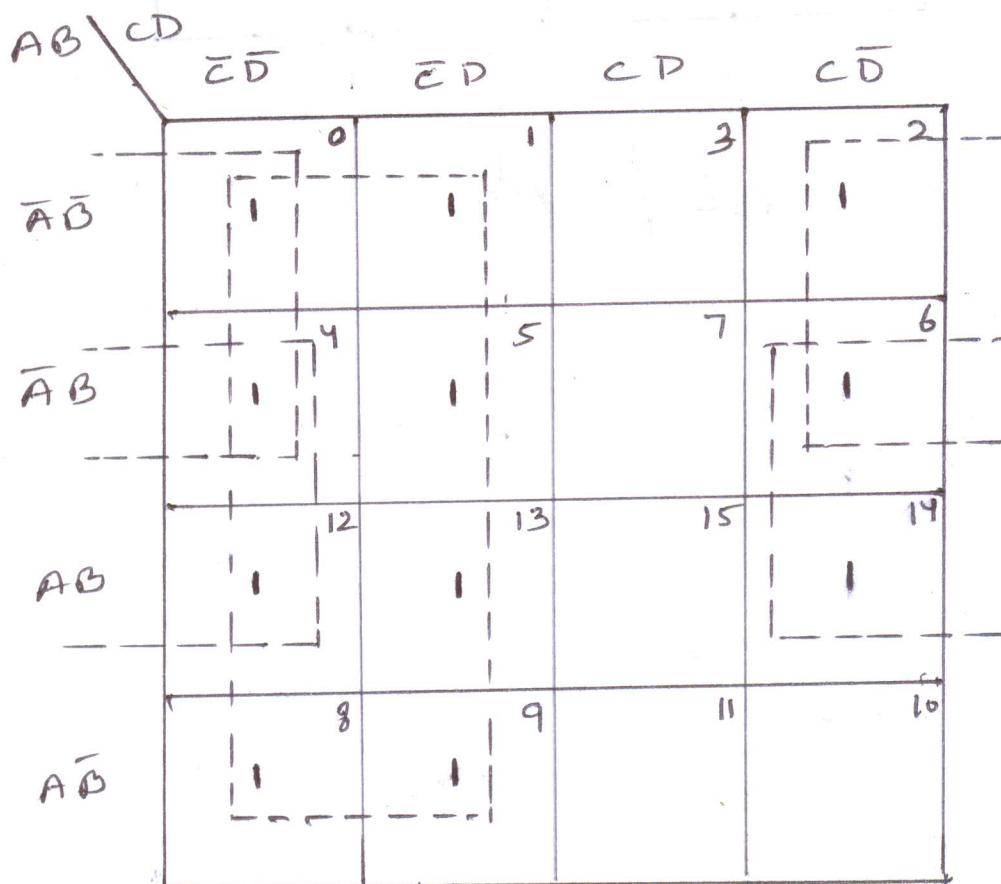(2) $Y(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$



$Y = \overline{C} + \overline{A}\overline{D} + B\overline{D}$
Ans

$$\textcircled{3} Y(A, B, C, D) = \sum m(0, 2, 4, 6, 7, 8, 10) \\ + \sum d(12, 14, 15)$$

AB \ CD		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2	
$\bar{A}B$	4	5	7	6	
AB	12	13	15	14	
$A\bar{B}$	8	9	11	10	

$$Y = \bar{D} + BC \quad \text{ANS.}$$

(4)

$$Y(A,B,C,D) = \sum m(0,1,2,12,13) + \sum d(8,9,10)$$

AB \ CD	CD			
	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0 1	1 1	3	2 1
$\bar{A}B$	4	5	7	6
AB	12 1	13 1	15	14
$AB\bar{B}$	8 X	9 X	11	10 X

$$Y = \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$$

Ans

Redundant group

Problems on K-map

$$1) Y = \sum m(1, 2, 3, 7) = B\bar{C} + AB + A\bar{C}$$

$$2) Y = \sum m(0, 3, 5, 6) = \bar{A}(\bar{B}\bar{C} + BC) + A(\bar{B}\bar{C} + \bar{B}C)$$

$$3) Y = \sum m(0, 1, 3, 5, 6, 7) = \bar{A}\bar{B} + AB + \bar{B}C$$

$$4) Y = \sum m(0, 1, 2, 3, 4, 6) = \bar{B} + \bar{C}$$

$$5) Y = \sum m(0, 1, 2, 4, 6) = \bar{B} + \bar{A}\bar{C}$$

$$6) Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C = \bar{A}B + \bar{A}\bar{C} + \bar{A}BC$$

$$7) Y = \sum m(1, 5, 7, 9, 11, 13, 15) = \bar{C}D + BD + AD$$

$$8) Y = \sum m(1, 3, 5, 9, 11, 13) = D(\bar{B} + \bar{C})$$

$$9) Y = \sum m(1, 3, 4, 5, 7, 9, 11, 13, 15) = Y = \bar{A}B\bar{C} + D$$

$$10) Y = \sum m(1, 2, 9, 10, 11, 14, 15) = \bar{B}(\bar{C}D + \bar{C}\bar{D}) + AC$$

$$11) Y = \sum m(4, 5, 8, 9, 11, 12, 13, 15) = \bar{C}(A+B) + AD$$

Redundant Group

$$12) Y = \sum m(1, 5, 6, 7, 11, 12, 13, 15) = \bar{A}\bar{C}D + \bar{A}BC + A\bar{B}\bar{C} + ACD$$

$$13) Y = \sum m(0, 1, 2, 5, 13, 15) = \bar{A}\bar{B}\bar{D} + ABD + \bar{A}\bar{C}D$$

$$14) Y = \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + A\bar{C} + \bar{B} \\ = \bar{B} + A\bar{C} + \bar{A}\bar{C}\bar{D}$$

Don't Care

$$15) Y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5) = CD + \bar{A}\bar{B}$$

$$16) Y = \sum m(1, 3, 11, 15) + d(0, 2, 5, 8, 14) = CD + \bar{A}\bar{B}$$

$$17) Y = \sum m(0, 2, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11) \\ = D + (AC + \bar{A}\bar{C})$$