

Problems related to half-wave and full-wave rectifier

1. A half-wave rectifier uses a diode with a forward resistance of $100\ \Omega$. If the input ac voltage is 220 V rms and local resistance is $2\text{ k}\Omega$. Determine:
(i) I_{max} , I_{dc} , and I_{rms} (ii) PIV (iii) load output voltage (iv) d.c. output power and a.c. input power (v) ripple factor (vi) TUF (vii) rectification efficiency.
Ans: (i) 148 mA, 47 mA, and 74 (ii) 311 V (iii) 94.32 V (iv) 4.45 W, 11.5 W (v) 1.21 (vi) 0.27 (vii) 38.6%
2. The load resistance of a centre tap full-wave rectifier is $500\ \Omega$ and secondary voltage is $60\sin(100\pi t)$. Calculate (i) peak, average and rms value of current (ii) ripple factor (iii) efficiency. Each diode has an idealized I-V characteristics having slope corresponding to a resistance of $50\ \Omega$.
Ans: (i) 0.109 A, 0.069 A and 0.077 A (ii) 0.482 (iii) 73.82%
3. A half-wave rectifier has a load resistance of $3.5\text{ k}\Omega$. If the diode and secondary of the transformer have a total resistance of $800\ \Omega$ and the input voltage has an a.c. signal of 240 V (peak value). Determine:
(i) peak, average and rms value of current (ii) d.c. output power (iii) a.c. input power (iv) efficiency (iii) ripple factor.
Ans: (i) 55.81 mA, 17.76 mA and 27.91 mA (ii) 1.1 W (iii) 3.35 W (iv) 32.85% (v) 1.21
4. A half-wave rectifier, having a diode of resistance $1000\ \Omega$ and load resistance of $1000\ \Omega$ rectifies an a.c. voltage of 310 V peak value. Calculate:
(i) peak, average and rms value of current (ii) d.c. output power (iii) a.c. input power (iv) efficiency
Ans: (i) 0.219 A, 0.07 A and 0.1096 A (ii) 4.868 W (iii) 24.02 W (iv) 20.26%
5. A full-wave rectifier uses a double diode with each element having a constant forward resistance of $500\ \Omega$. The transformer rms secondary voltage from the centre tap to each plate is 300 V , the load resistance of $2.5\text{ k}\Omega$. Determine:
(i) dc out power and ac input power (ii) efficiency.
Ans: (i) 20.3 W and 30 W (ii) 67.67 %
6. A single wave full-wave rectifier uses two diodes the internal resistance of each being $20\ \Omega$. The transformer rms secondary voltage for centre tap to each of the secondary is 50 V and load resistance is $980\ \Omega$. Determine:
(i) mean load current (ii) rms load current (iii) efficiency
Ans: (i) 45 mA (ii) 50 mA (iii) 79.58%
7. The turn ratio of a transformer used in a half-wave rectifier is 10:1. The primary is connected to the power mains 220 V . The diode resistance in forward bias is $5\ \Omega$. The load resistance is $10\text{ k}\Omega$. Determine:
(i) dc output voltage, (ii) rms output voltage, (iii) TUF (iv) Rectification efficiency.
8. An a.c. supply of 230 V is applied to a half wave rectifier circuit through a transformer of turn ratio 10:1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal.
Ans: (i) 10.36 V (ii) 32.35
9. A crystal diode having internal resistance $r_f = 20\ \Omega$ is used for half wave rectification. If applied voltage $v = 50\sin \omega t$ and load resistance $R_L = 800\ \Omega$, find:
(i) I_m , I_{dc} , I_{rms} (ii) a.c. power input and d.c. power output (iii) d.c. output voltage (iv) efficiency
Ans: (i) 61 mA, 19.4 mA, 30.5 mA (ii) 0.763 W, 0.301 W (iii) 15.52 V (iv) 39.5%
10. A half wave rectifier is used to supply 50 V d.c. to a resistance load of $800\ \Omega$. The diode has a resistance of $25\ \Omega$. Calculate a.c. voltage required.
Ans: maximum voltage required $V_m = 162\text{ V}$
11. A full wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at $20\ \Omega$. The transformer rms secondary voltage from center tap to each end of secondary is 50 V and load resistance of $980\ \Omega$. Find:
(i) the mean load current (ii) the rms value of load current
Ans: (i) 45 mA (ii) 50 mA

12. A full wave rectifier uses two ideal diodes. The turn ratio of a transformer used is 5:1. The primary is connected to the power mains 230V and load resistance of 100Ω . Find:
(i) d.c. output voltage (ii) PIV (iii) rectification efficiency
Ans: (i) 20.7V (ii) 65 V (iii) 81.2%
13. A half wave bridge rectifier uses four ideal diodes. The turn ratio of a transformer used is 4:1. The primary is connected to the power mains 230V, 50Hz and load resistance of 200Ω . Find:
(i) d.c. output voltage (ii) PIV (iii) output frequency
Ans: (i) 52V (ii) 81.3V (iii) 100Hz
14. The four diode used in a bridge rectifier circuit have forward resistance which may be considered constant at 1Ω and infinite reverse resistance. The alternating supply voltage is 240 V r.m.s. and load resistance is 480Ω . Calculate (i) mean load current (ii) power dissipated in each load.
Ans: (i) 0.45 A (ii) 0.123 W