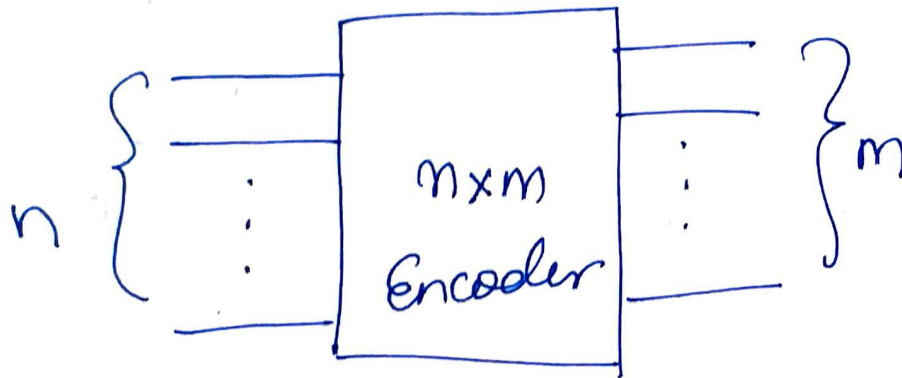


Introduction to Encoders & Decoders


↳ They are combinational circuits.

↳ Encoders have " n " inputs & " m " outputs.


↳ Function of decoder is opposite to encoder.



↳ Encoder

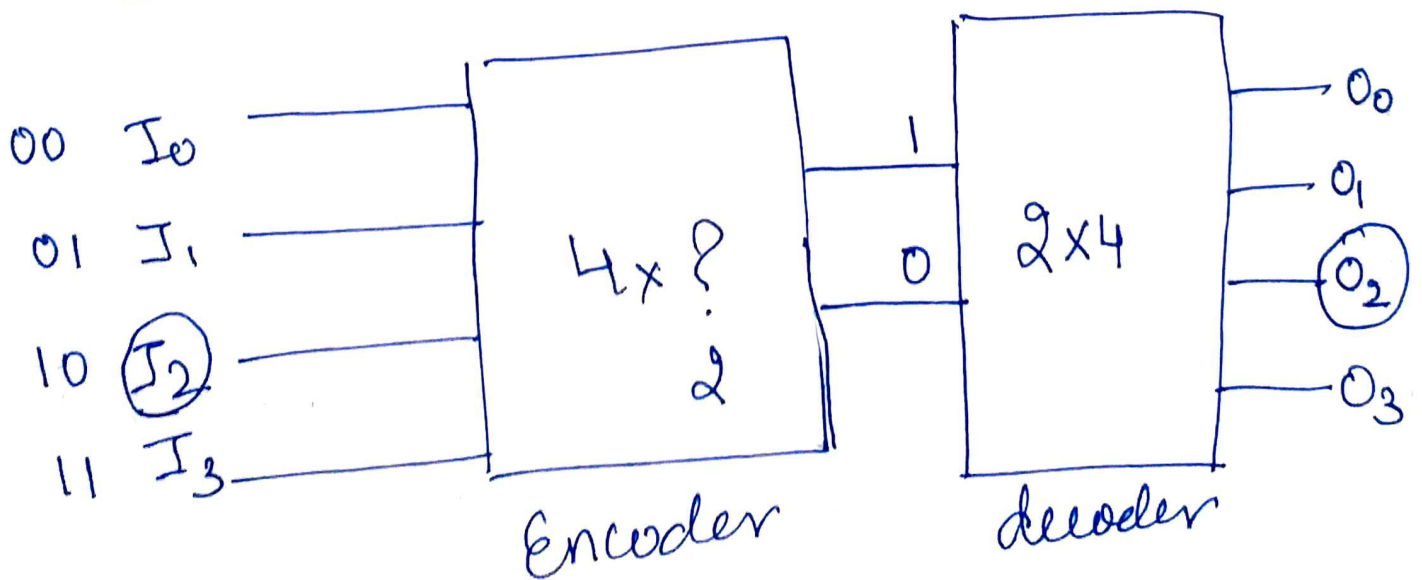

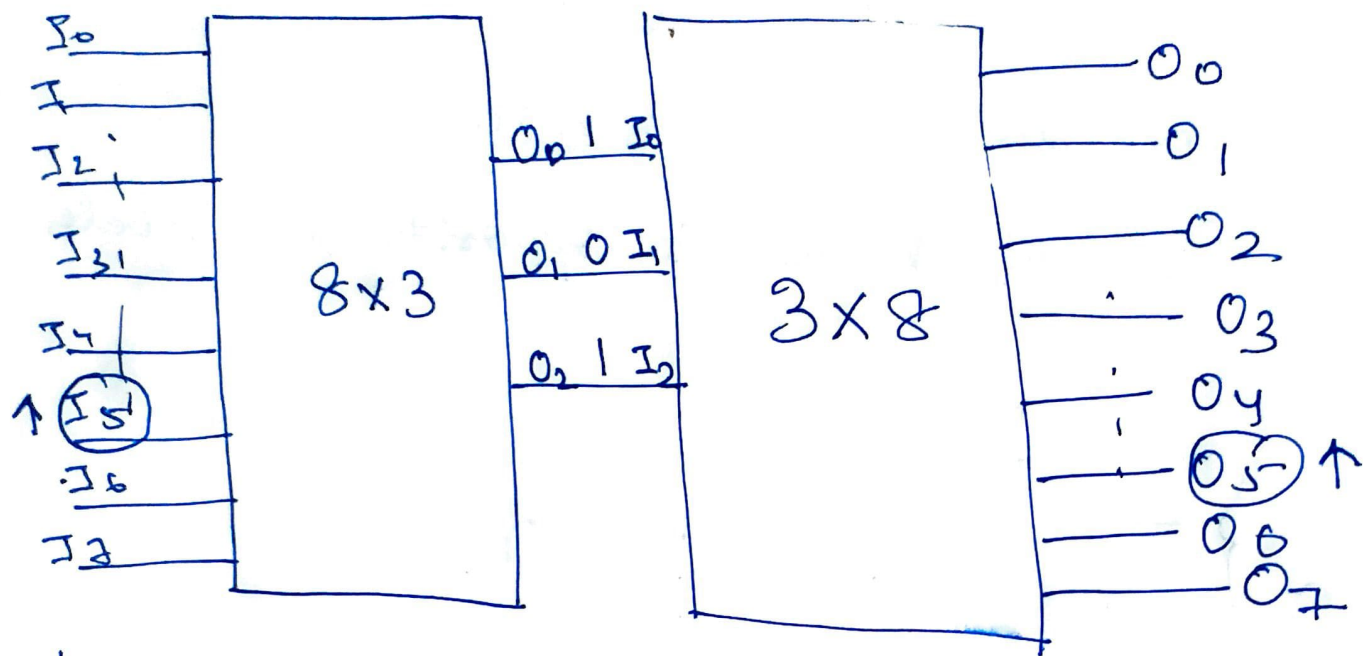$n = 4$
 $n = 2^m \rightarrow m$ } Encoder & decoder is reverse.
↳ no. of o/p



→ Appln

Express Boolean Expression by reducing the connections.

Types of Encoder

i) Priority Encoder


* If more than one I/P is high, the priority has to be given (smallest priority or largest priority).

2) Decimal to BCD.

3) Octal to binary

4) Hex to binary.

Priority Encoder

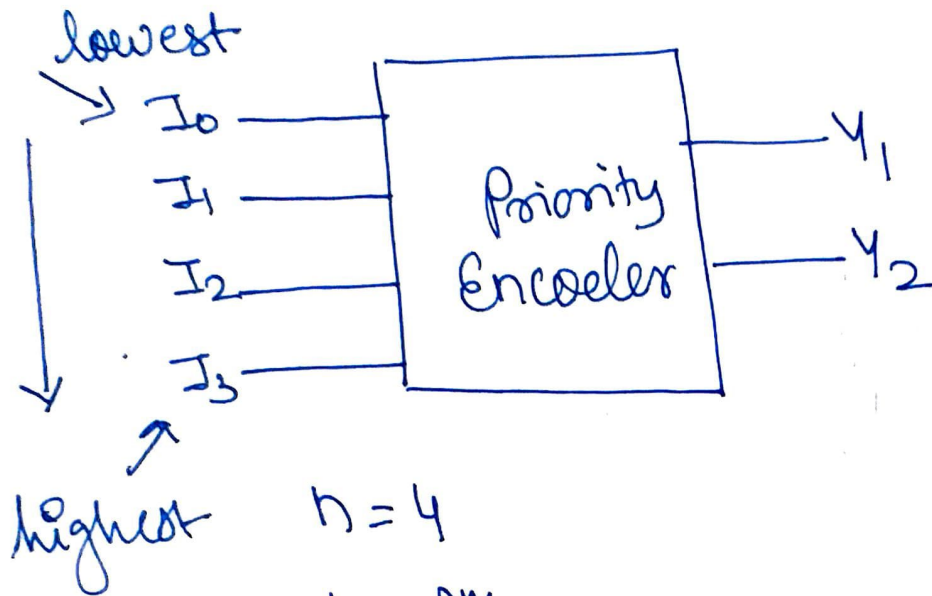

$$n = 4$$


$$n = 2^m$$

$$m = 2$$


↳ $I_3 \uparrow \rightarrow Y_1 = 1, Y_2 = 1$

I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	x	0	1
0	1	x	x	1	0
1	x	x	x	1	1

g K-Map

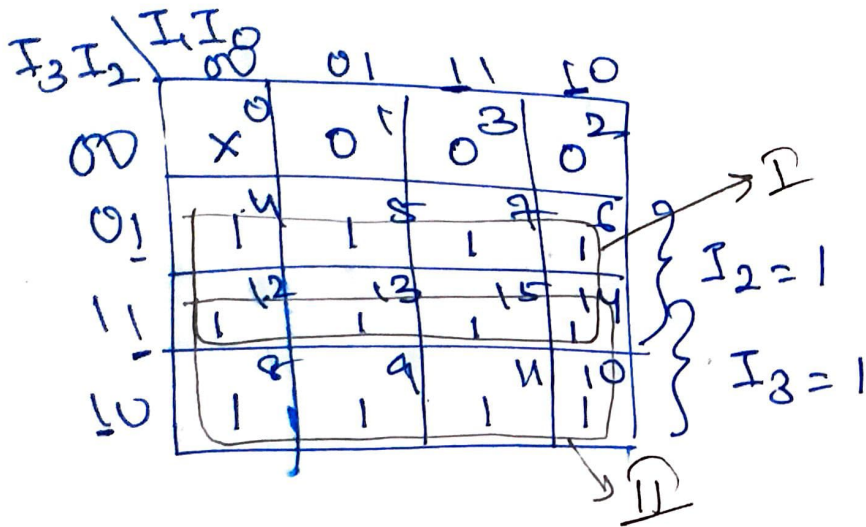


$$Y_1 = I_2 + I_3$$

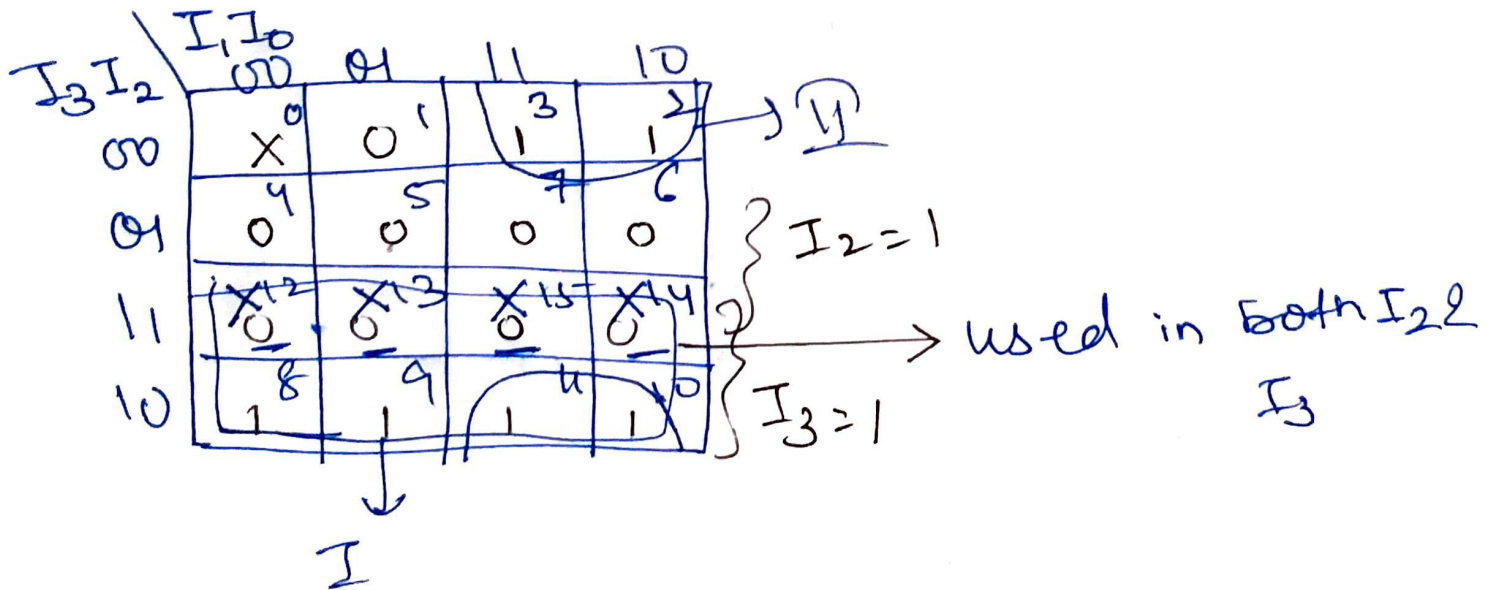

$$Y_0 = I_3 + I_1 \overline{I_2}$$

Decimal to BCD

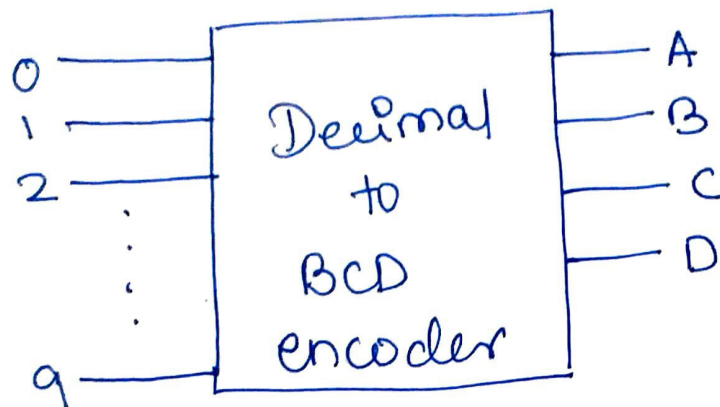

decimal Input	BCD			
	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

Annotations from the image:

- A box around inputs 2 and 3 with an arrow pointing to B: $B=1$
- A box around inputs 4, 5, 6, and 7 with an arrow pointing to C: $C=1$
- A box around inputs 6 and 7 with an arrow pointing to B: $\rightarrow B=1$
- A box around inputs 8 and 9 with an arrow pointing to D: $D=1$

$$D = 8 + 9$$

$$C = 4 + 5 + 6 + 7$$

$$B = 2 + 3 + 6 + 7$$

$$A = 1 + 3 + 5 + 7 + 9$$

